



The impedance value of a power amplifier as seen from the power supply is typically low and mostly resistive in nature. Its value can be approximated by the amplifier's load impedance.

```
.ac dec 100 10 20k
.step param Load list 8 32
```